

Student Name	Lin Rui
Maynooth ID	21124264

Student Name	林锐
FZU ID	832103316

## CS220 Computer Architecture

### Practical 2 Report

#### Part A


- a. Design a circuit that bases on the function  $f(A,B,C,D) = \sum m(0,4,5,8,9,10,12)$ .
- b. The relevant truth table, k-map, and minimal Sum-of-Products expression

A	B	C	D	f
0	0	0	0	1
0	0	0	1	0
0	0	1	1	0
0	0	1	0	0
0	1	0	0	1
0	1	0	1	1
0	1	1	1	0
0	1	1	0	0
1	0	0	0	1
1	0	0	1	1
1	0	1	1	1
1	0	1	0	0
1	1	0	0	1
1	1	0	1	0
1	1	1	1	0
1	1	1	0	0

AB \ CD	00	01	11	10
00	1	1	1	1
01	0	1	0	1
11	0	0	0	0
10	0	0	0	1

$$f = \overline{C}\overline{D} + \overline{A}B\overline{C} + A\overline{B}\overline{D} + A\overline{B}\overline{C}$$

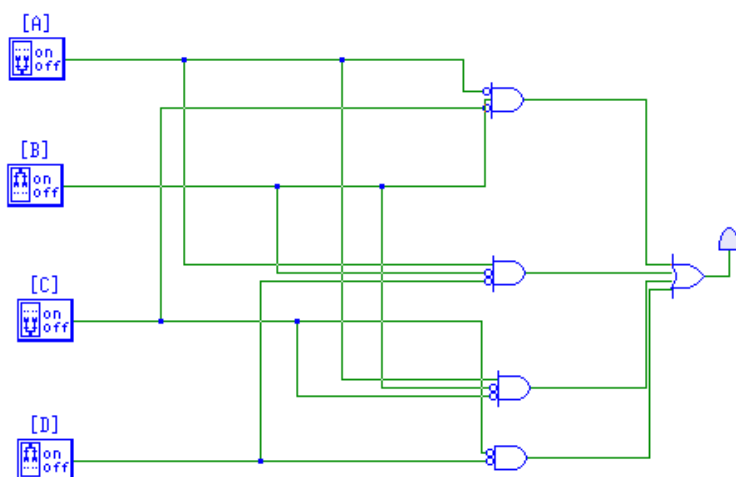
- c. Implement the function on the simulator



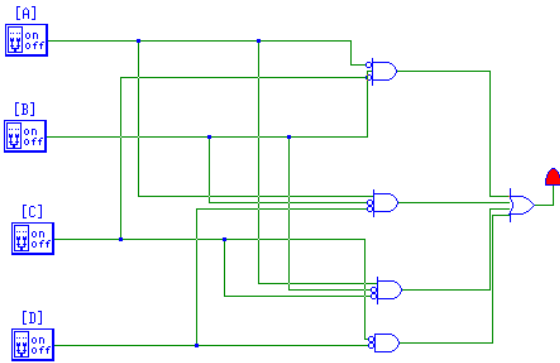
- d. Verification of Experiment and Observations

The circuit worked in accordance with the truth table for all input combinations.


e.g.,1  $m_0: \bar{A}\bar{B}\bar{C}\bar{D} = 1$



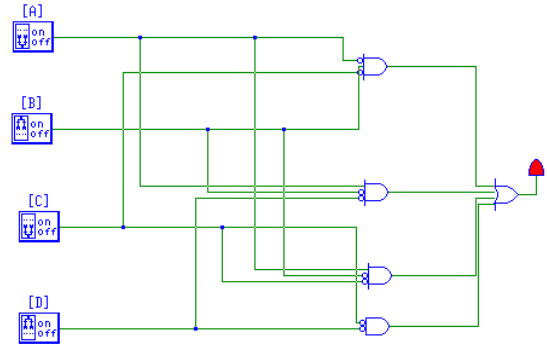
e.g.,2  $m_9: \bar{A}\bar{B}\bar{C}D = 1$



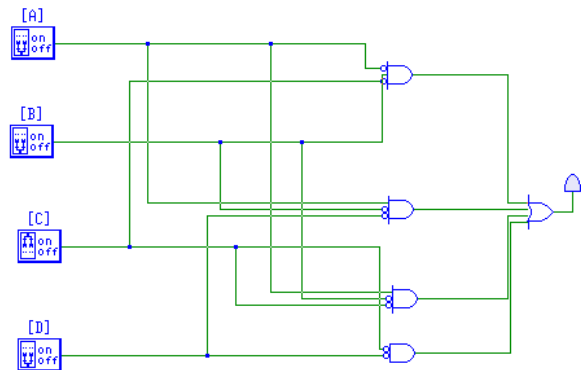e.g.,3  $m_4: \bar{A}\bar{B}C\bar{D} = 0$



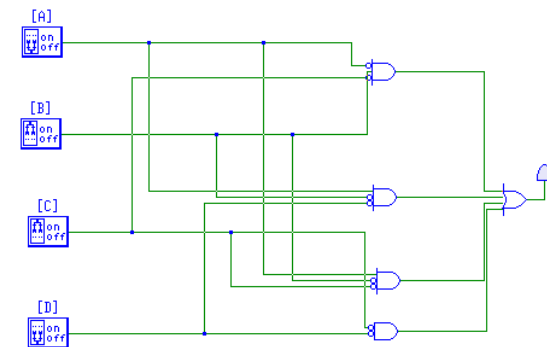e.g.,4  $m_7: \bar{A}B\bar{C}\bar{D} = 0$



## Part B

a. Design a 1-bit full adder circuit using only five two-input logic gates.

b. The relevant truth table and k-maps.

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


X \ Y	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$C = XY + YZ + XZ$

X \ Y	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$S = \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z + XYZ + X\bar{Y}\bar{Z} = X \oplus Y \oplus Z$

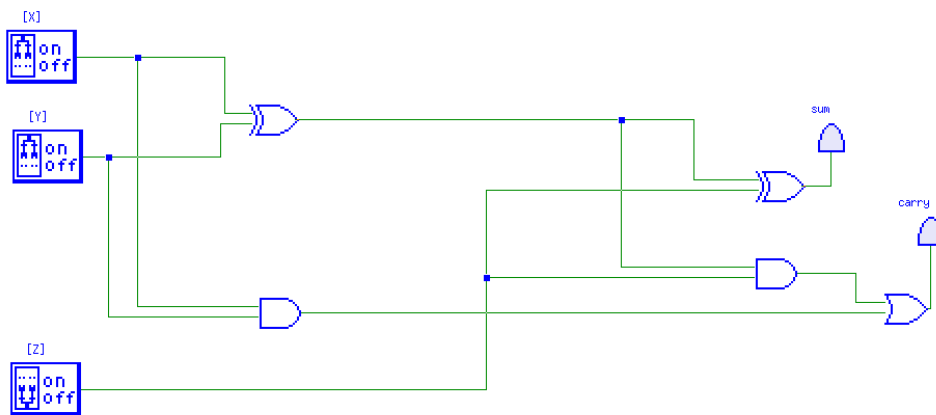
c. Implement the function on the simulator



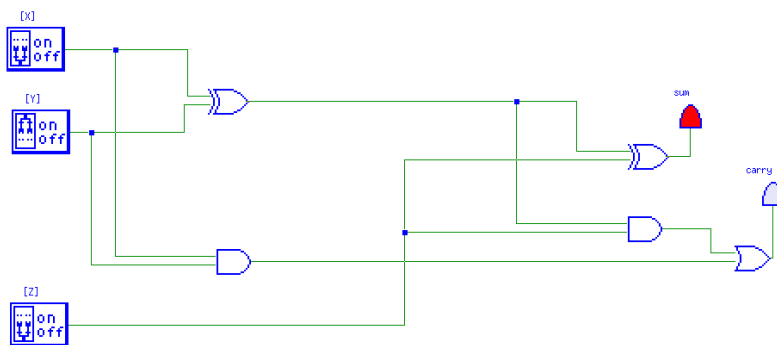d. Verification of Experiment and Observations

The circuit worked in accordance with the truth table for all input combinations.

e.g.,1  $X = 0, Y = 1, Z = 0, C = 0, S = 1$



e.g.,2  $X = 1, Y = 1, Z = 0, C = 1, S = 0$

