

Student Name	Lin Rui
Maynooth ID	21124264


Student Name	林锐
FZU ID	832103316

# CS220 Computer Architecture

## Practical 5 Report

### Part A

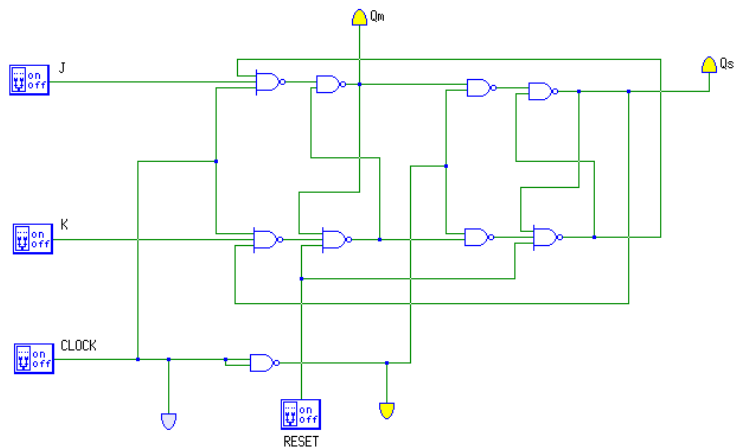a. Implement a Master–Slave J–K flip–flop circuit on the simulator.



b. The flip–flop obeys the truth table given below.




<i>J</i>	<i>K</i>	<i>Q<sub>n</sub></i>	<i>Q<sub>n+1</sub></i>	<i>Description</i>
0	0	0	0	No change
		1	1	
0	1	0	0	Reset
		1	0	
1	0	0	1	Set
		1	1	
1	1	1	0	Toggle
		0	1	

c. Verification of Experiment and Observations




The three screenshots in one case corresponds to the change of *Q* during one clock pulse period.







$$J = 0, K = 0$$

$$Q = 0, Q_{n+1} = 0$$

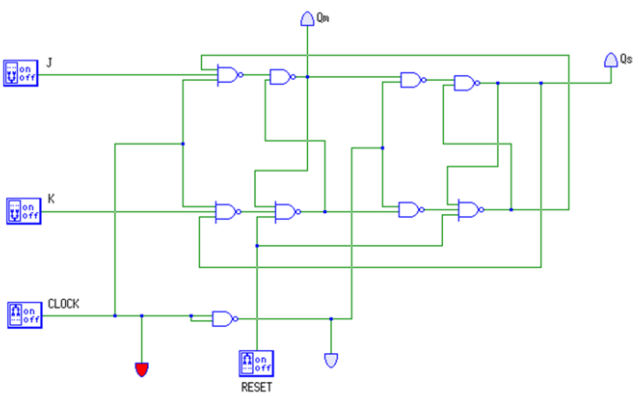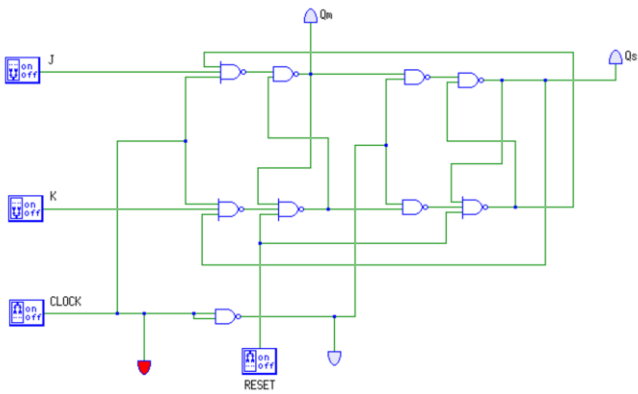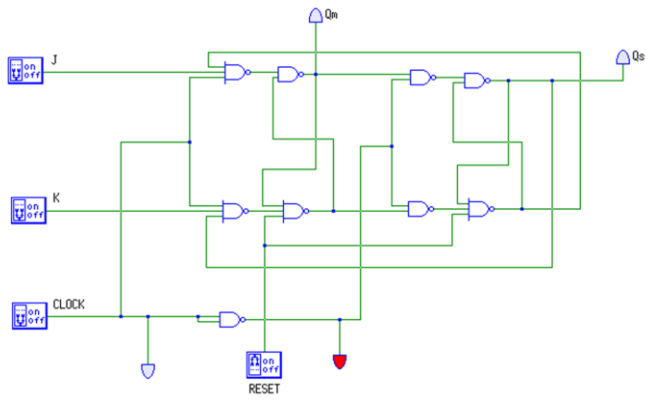




$$Q = 1, Q_{n+1} = 1$$

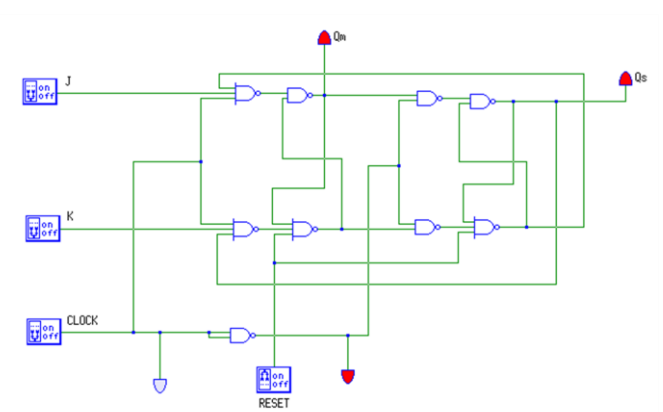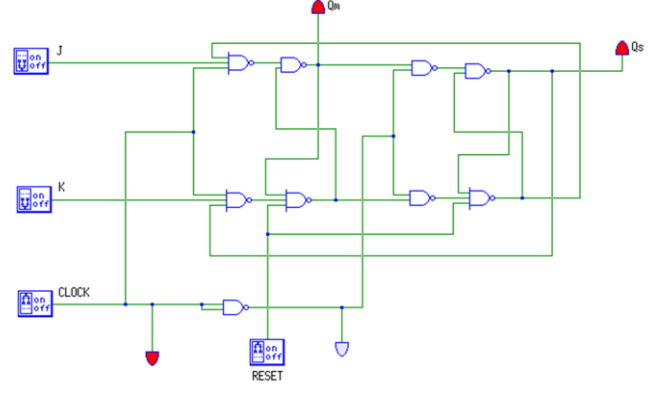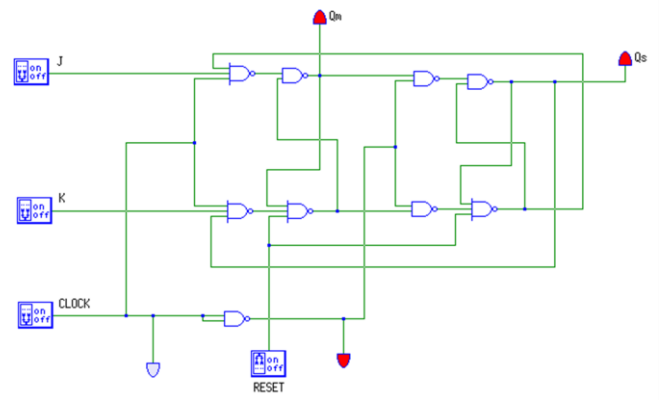

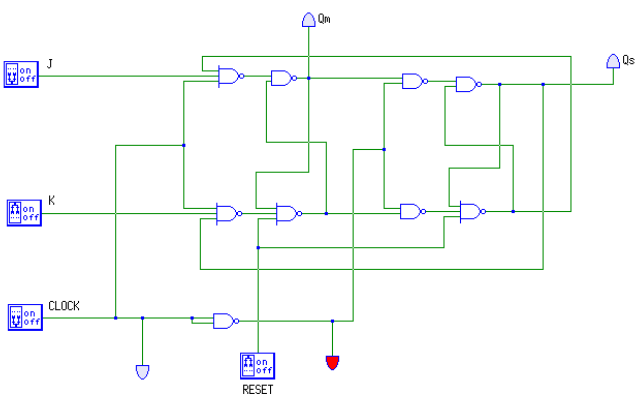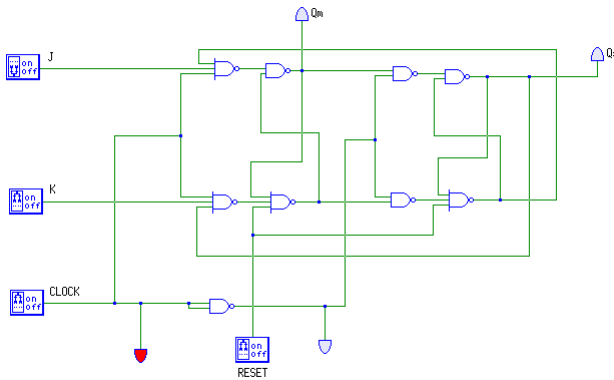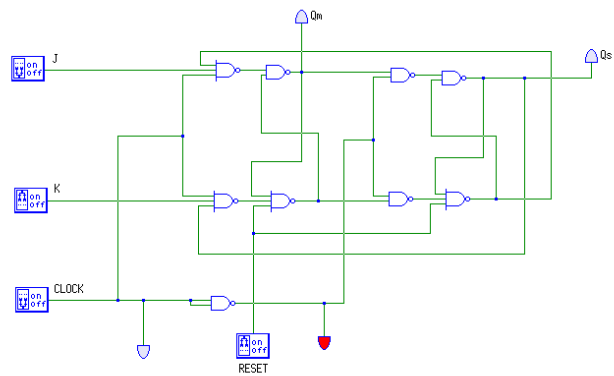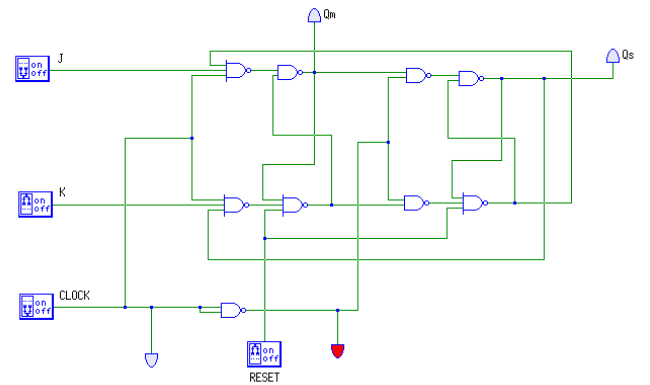
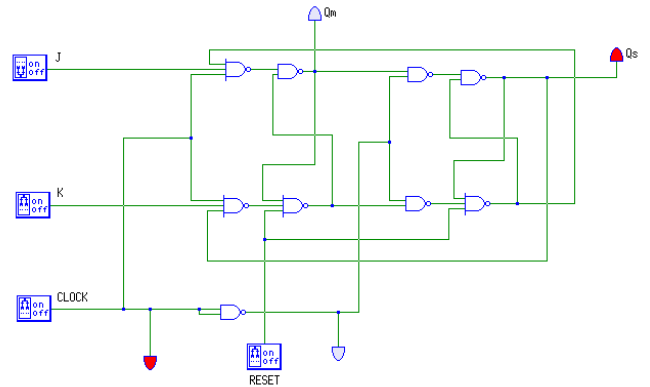
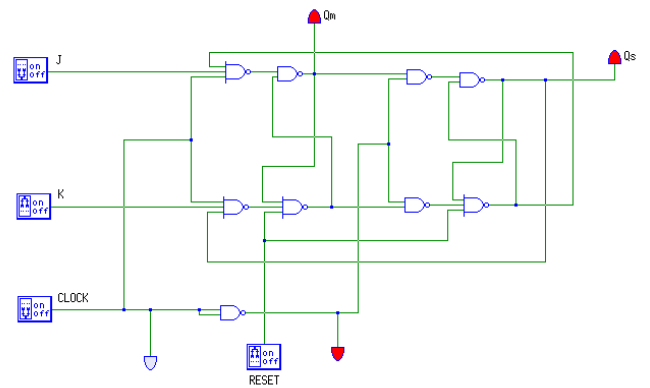
$$J = 0, K = 1$$
$$Q = 0, \quad Q_{n+1} = 0$$

$$Q = 1, \quad Q_{n+1} = 0$$


$J = 1, K = 0$

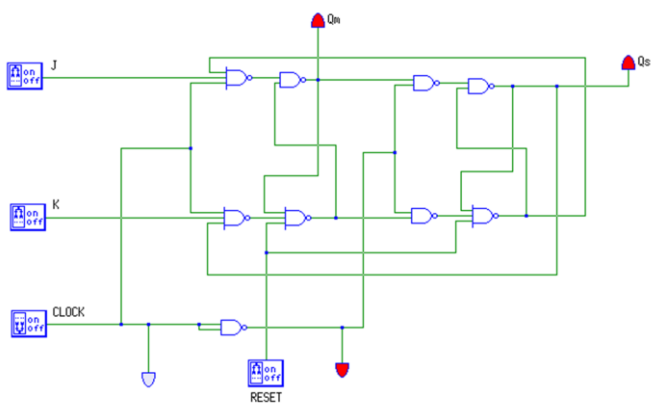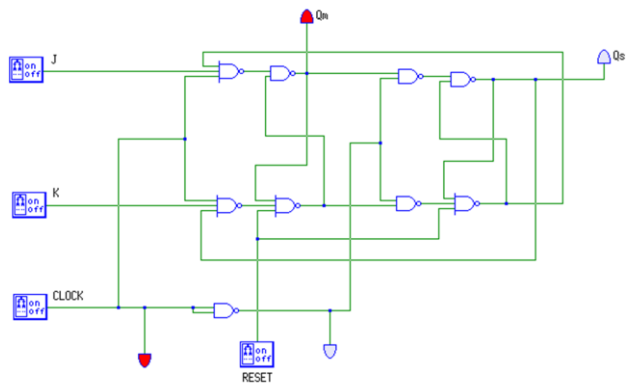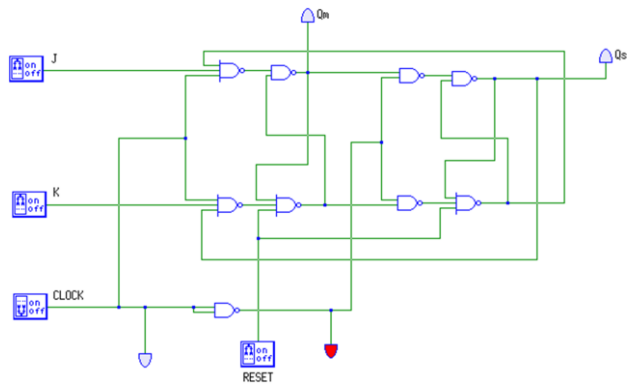$Q = 0, Q_{n+1} = 1$

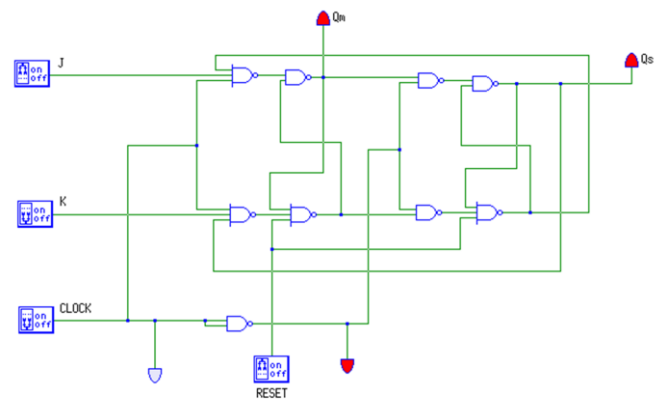
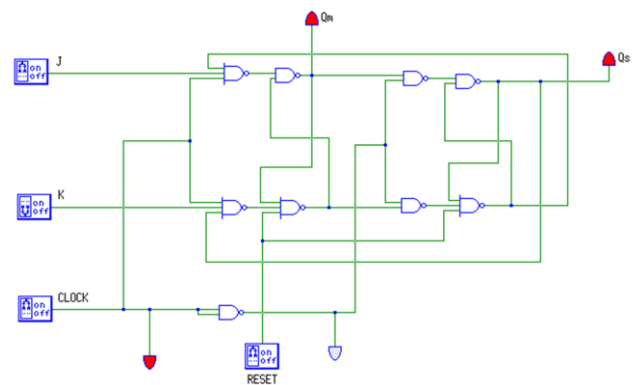
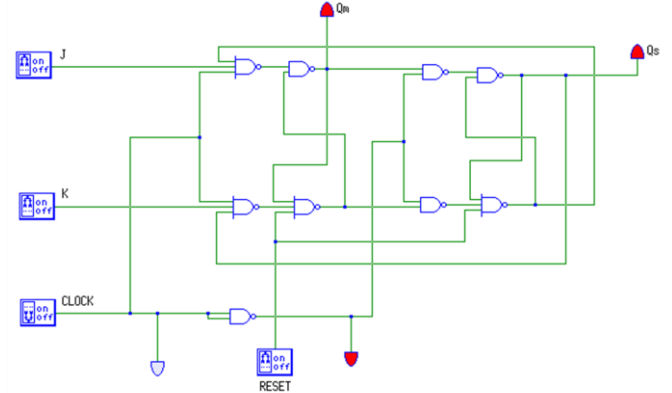


$Q = 1, Q_{n+1} = 1$






$$J = 1, K = 1$$

$$Q = 0, Q_{n+1} = 1$$

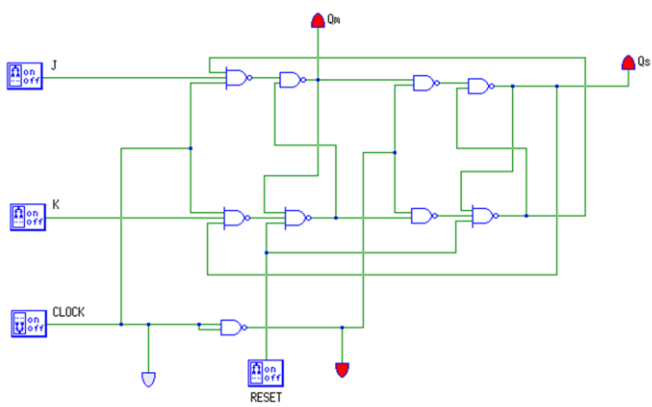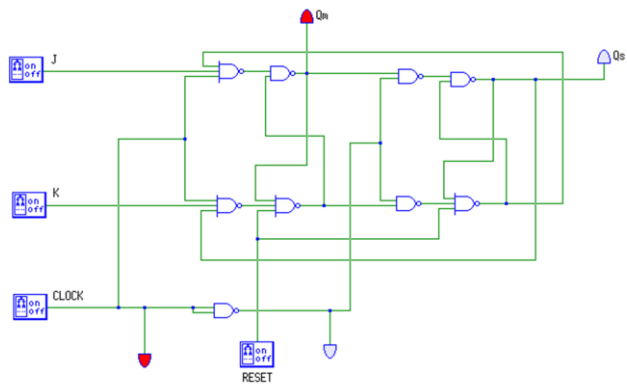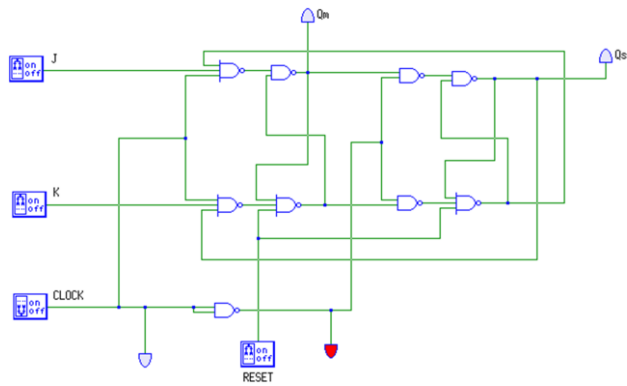


$$Q = 1, Q_{n+1} = 0$$

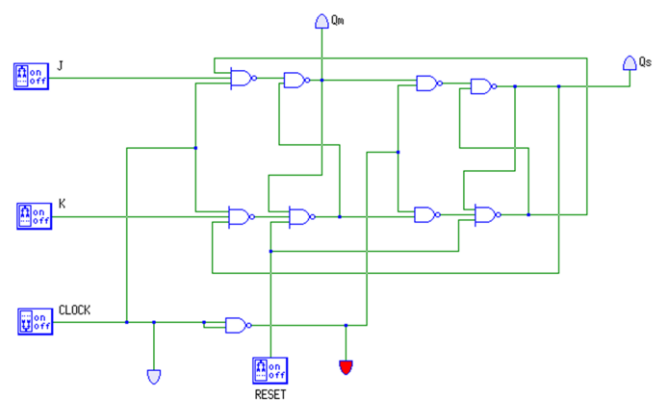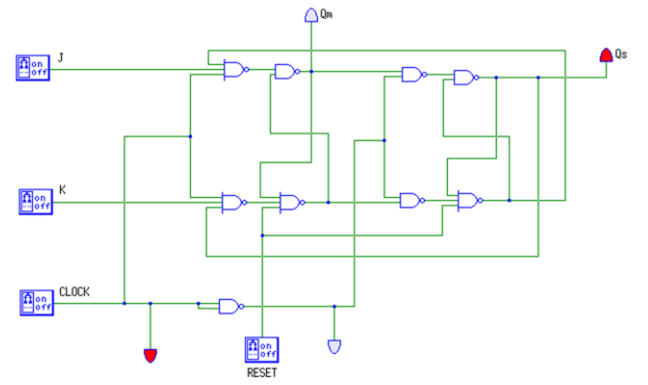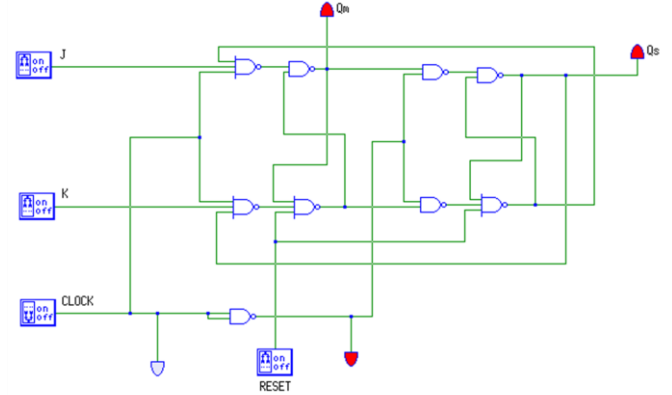

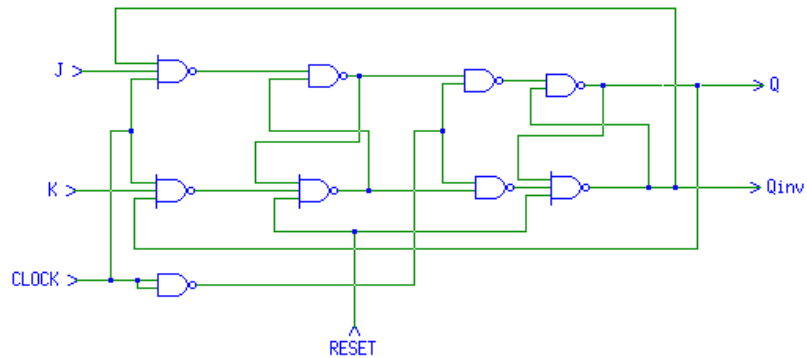
## Part B

- Construct a Master–Slave J–K flip–flop circuit Modules in TKGate.
- Edit Module Implementations.



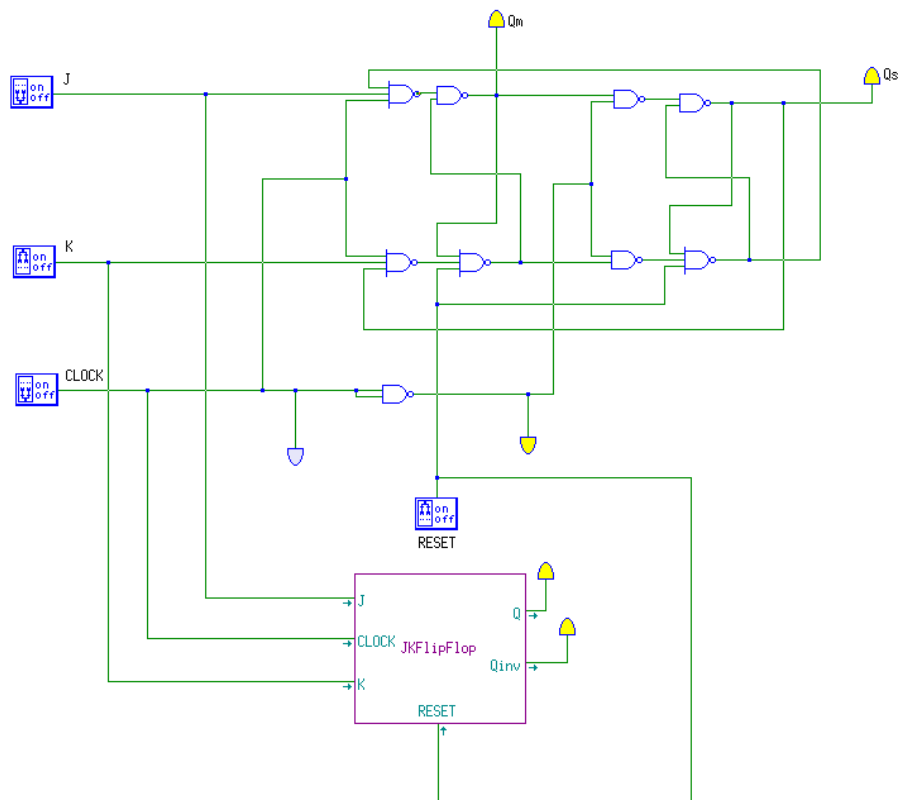
- Use User Defined Modules combined with the circuit used in part A.




- Verification of Experiment and Observations

The flip–flop Qs is as the same as the module Q output for different input combinations. Here are two examples in all cases.

e.g.,1  $J = K = 0, Q = Q_s = 0$

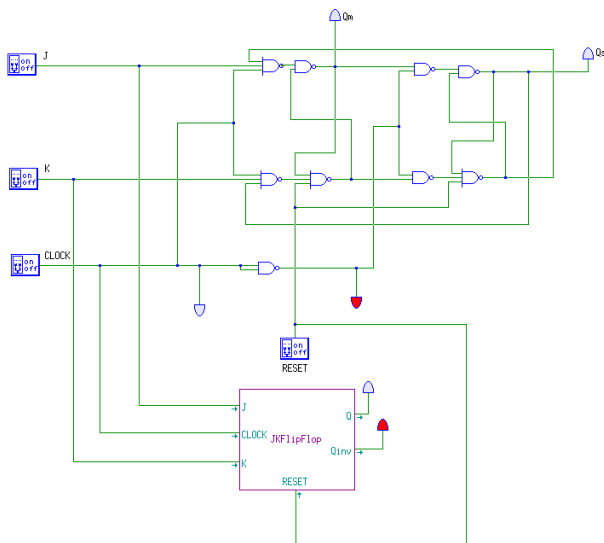


e.g.,2  $J = 1, K = 0, Q = Q_s = 1$

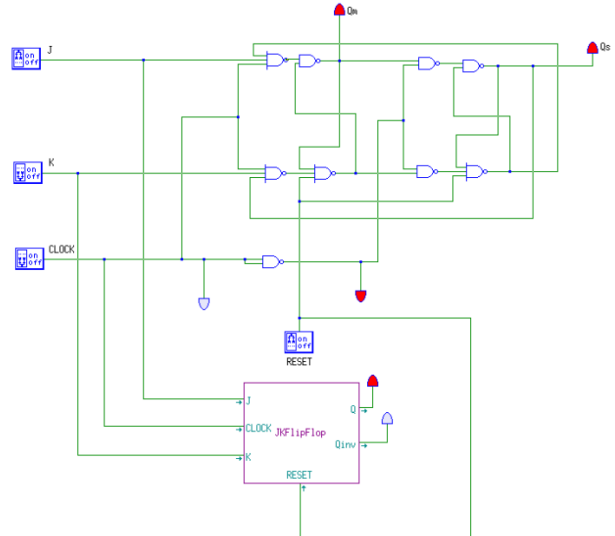


## Part C

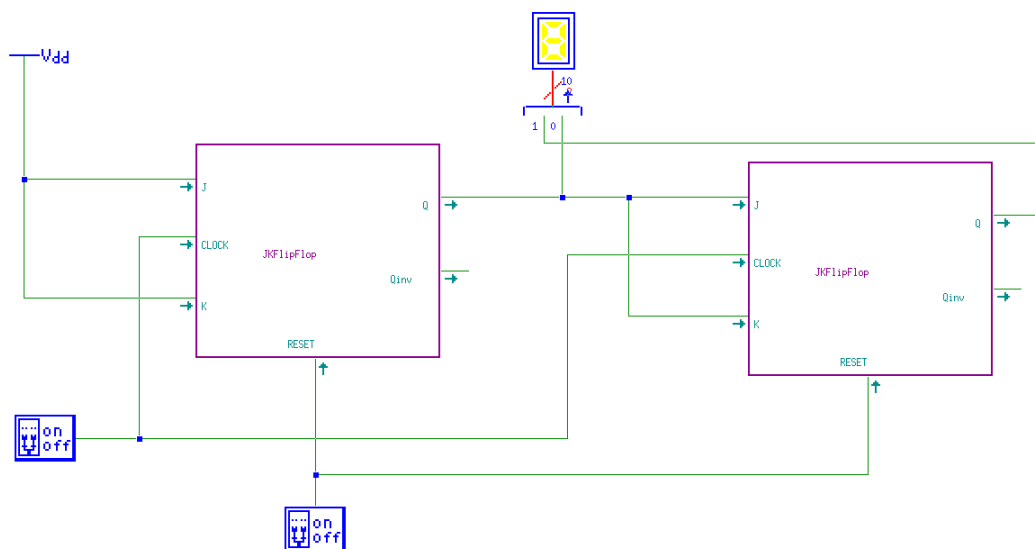- a. Implement a 2-bit synchronous counter using two instances of the module used in part B. The output of the counter should be displayed on a decimal counter.




- b. Verification of Experiment and Observations

Count = 0

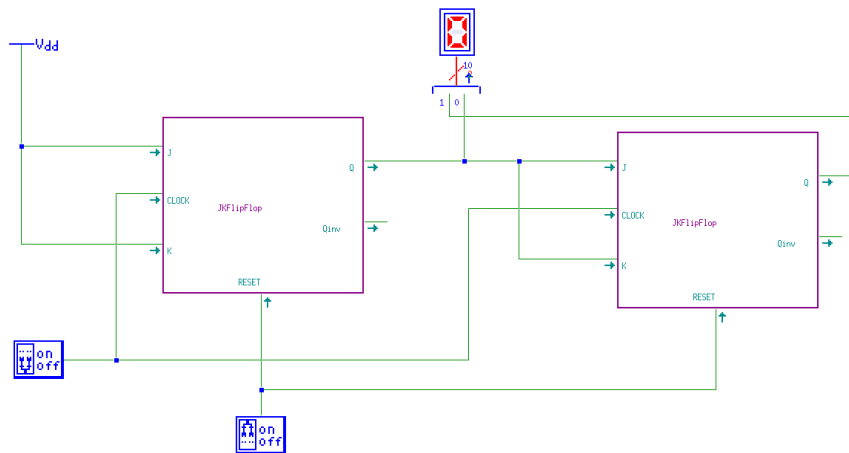

Count = 1

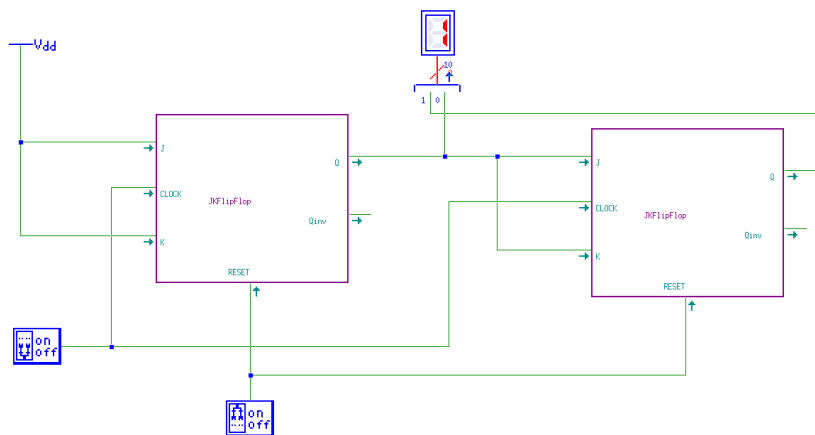

Count = 2

