

<i>Student Name</i>	Lin Rui
<i>Maynooth ID</i>	21124264

<i>Student Name</i>	林锐
<i>FZU ID</i>	832103316

CS220 Computer Architecture

Practical 8 Report


Circuit description

A synchronous sequential circuit as a 3-bit left shift register.

- Using the J-K flip-flop module.
- Displaying the value of its contents in decimal.

Design Details

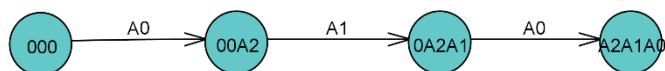1. Construct a transition diagram and table.



Q_2^n	Q_1^n	Q_0^n	<i>Input/X</i>	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}
0	0	0	A2	0	0	A2
0	0	A2	A1	0	A2	A1
0	A2	A1	A0	A2	A1	A0

2. Derive Boolean expressions.

$$Q_0^{n+1} = X = X(Q_0^n + \overline{Q_0^n}) = X\overline{Q_0^n} + XQ_0^n$$

$$\begin{cases} J_0 = X \\ K_0 = \overline{X} \end{cases}$$

$$Q_1^{n+1} = Q_0 = Q_0(Q_1^n + \overline{Q_1^n}) = Q_0\overline{Q_1^n} + Q_0Q_1^n$$

$$\begin{cases} J_1 = Q_0 \\ K_1 = \overline{Q_0} \end{cases}$$

$$Q_2^{n+1} = Q_1 = Q_1(Q_2^n + \overline{Q_2^n}) = Q_1\overline{Q_2^n} + Q_1Q_2^n$$

$$\begin{cases} J_2 = Q_1 \\ K_2 = \overline{Q_1} \end{cases}$$

Circuit schematic

